




## Data acquisition from a photodiode

---

# Photodiodes

- Photodiodes are semiconductor devices with PN or PIN structure typically used as radiant power transducers
- The energy transferred by the electromagnetic radiation, absorbed in the depletion or in the intrinsic region is responsible for the generation of electron/hole pairs, eventually contributing to the formation of a current
- The voltage/current characteristic of a photodiode is therefore the same as in a diode, with the addition of a photo-generated current term  $I_{ph}$

$$I_D = I_0(e^{V_D/V_T} - 1) - I_{ph}$$

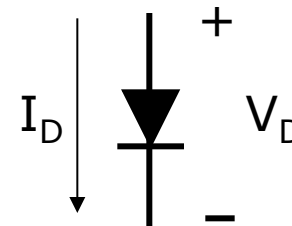

where  $I_0$  is the diode leakage current,  $V_D$  is the voltage across the device and  $V_T$  is the thermal voltage. Note that, in reverse bias operating conditions ( $V_D < 0$ ), the first term in the expression reduces to  $I_0$ , while for  $V_D = 0$ ,  $I_D = -I_{ph}$ .



# Photodiodes

- The photo-generated current  $I_{ph}$  is proportional to the incident radiant power, i.e., to the flux of photons hitting the device:

$$I_{ph} = S \cdot P = \frac{\eta e}{h \nu} P, \quad \frac{P}{h \nu} = \# \text{ fotoni al sec.}$$

- where  $S$  is the spectral (or radiometric) sensitivity,  $\eta$  is the quantum efficiency,  $e$  is the elementary charge ( $1.602 \cdot 10^{-19} \text{ C}$ ),  $P$  is the power of the incident electromagnetic wave,  $h$  is the Plank's constant ( $6.625 \cdot 10^{-34} \text{ J}\cdot\text{s}$ ) and  $\nu$  is the electromagnetic wave frequency
- Other characteristic parameters of a photodiode are the linearity, the dark current, the junction capacitance, the breakdown voltage and the response time



# Main uses of thermistors

Application field	Use or device
Cameras	Light intensity measurement, automatic control of the shutter, auto-focus, flash unit control
Medical instrumentation	TAC scanner, X-ray detection, biological analysis (e.g., blood), oximetry
Safety devices	Smoke and flame detectors, X-ray systems for airplane inspection, intrusion detectors
Automotive	Headlight dimmer, sun light detector (for air conditioning)
Communications	Opto-electronic converters, remote optical control
Industry	Bar code readers, encoders, position detectors, toner density measurement in printers



# Purpose of the experiment

- Implement a system for data acquisition from a radiant power transducer, in particular from a photodiode. The system should include
  - a conditioning circuit for the signal coming from the photodiode
  - a virtual instrument implemented in the LabView programming environment serving as an interface between the acquisition system and the user
- The virtual instrument should take care of acquiring the room radiant power and representing the time evolution of the measured voltage and the instantaneous value of the radiant power




# Operating modes for the photodiode

**Photovoltaic mode:** the photodiode is operated with no bias voltage applied and can supply electrical power (in the passive sign convention,  $V_D I_D < 0$ , with  $I_D \leq 0$  and  $V_D > 0$ ); in particular, for  $I_D = 0$ , the photodiode behaves like a voltage source



$$V_D = V_T \ln \left( \frac{I_{ph}}{I_0} + 1 \right)$$

**Photoconductive mode:** the photodiode is operated in reverse or zero volt bias conditions,  $V_D \leq 0$ , and behaves like a current source; in particular, if the potential difference across the device is close to zero


$$I_D = -I_{ph}$$

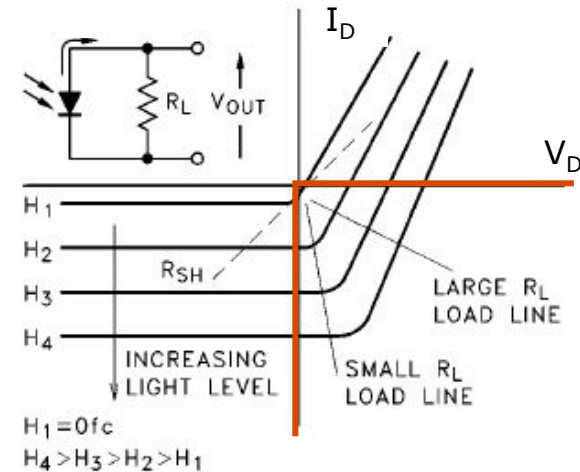

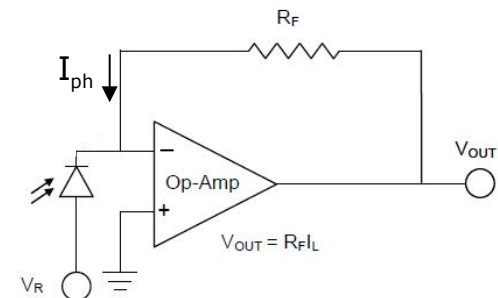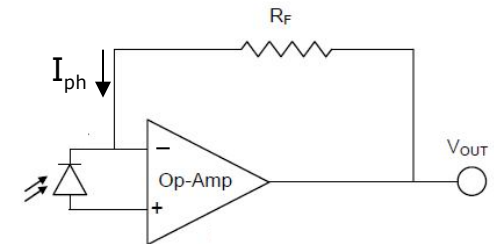Current/Voltage Characteristics - Photovoltaic Mode



# Conditioning circuit

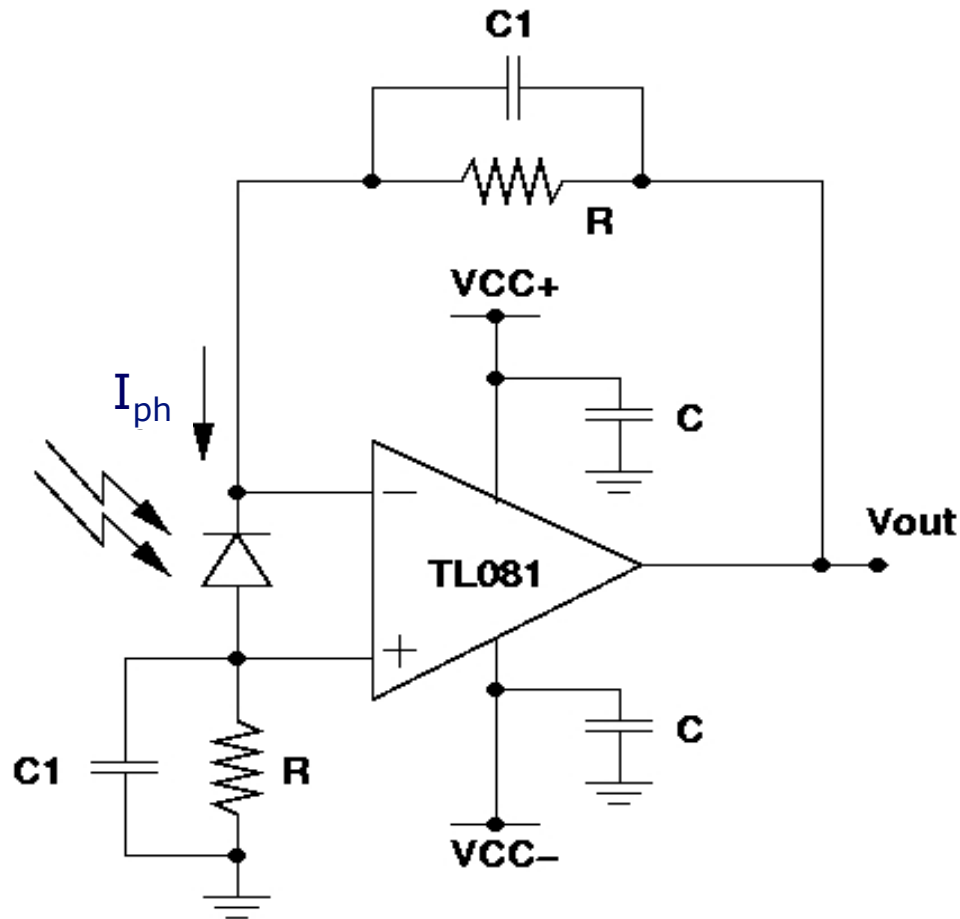

- $R=1\text{ M}\Omega$
- $C=100\text{ nF}$
- $C1=15\text{ nF}$
- $VCC+=+15\text{ V}$
- $VCC-=-15\text{ V}$
- PD: VTB8440B

# Conditioning circuit

- The proposed scheme, in principle, makes it possible to cancel the dark current contribution (current flowing through the diode when  $V_D=0$ )

$$V_{\text{out}} = 2 \cdot R \cdot I_{\text{ph}} = 2 \cdot S \cdot R \cdot P$$

voltage at the amplifier output

spectral sensitivity

incident light power


- Another advantage of the proposed conditioning circuit lies in the reduction of the effects of the input bias currents on the output of the operational amplifier

$$V_{\text{out}} \big|_{I^+, I^-} = -I^+R + I^-R = -R\Delta I$$

where  $\Delta I = I^+ - I^-$  is the offset of the input bias currents of the operational amplifier



# TL081 JFET input OpAmp

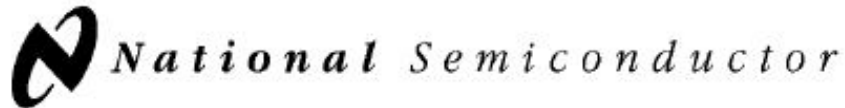

December 1995

## TL081 Wide Bandwidth JFET Input Operational Amplifier

### General Description

The TL081 is a low cost high speed JFET input operational amplifier with an internally trimmed input offset voltage (BI-FET II™ technology). The device requires a low supply current and yet maintains a large gain bandwidth product and a fast slew rate. In addition, well matched high voltage JFET input devices provide very low input bias and offset currents. The TL081 is pin compatible with the standard LM741 and uses the same offset voltage adjustment circuitry. This feature allows designers to immediately upgrade the overall performance of existing LM741 designs.

The TL081 may be used in applications such as high speed integrators, fast D/A converters, sample-and-hold circuits and many other circuits requiring low input offset voltage, low input bias current, high input impedance, high slew rate and wide bandwidth. The devices has low noise and offset voltage drift, but for applications where these requirements


are critical, the LF356 is recommended. If maximum supply current is important, however, the TL081C is the better choice.

### Features


■ Internally trimmed offset voltage	15 mV
■ Low input bias current	50 pA
■ Low input noise voltage	25 nV/ $\sqrt{\text{Hz}}$
■ Low input noise current	0.01 pA/ $\sqrt{\text{Hz}}$
■ Wide gain bandwidth	4 MHz
■ High slew rate	13 V/ $\mu\text{s}$
■ Low supply current	1.8 mA
■ High input impedance	$10^{12}\Omega$
■ Low total harmonic distortion $A_V = 10$ , $R_L = 10\text{k}$ , $V_O = 20\text{ Vp-p}$ , $\text{BW} = 20\text{ Hz} - 20\text{ kHz}$	<0.02%
■ Low 1/f noise corner	50 Hz
■ Fast settling time to 0.01 %	2 $\mu\text{s}$

# TL081 JFET input OpAmp


Typical Connection

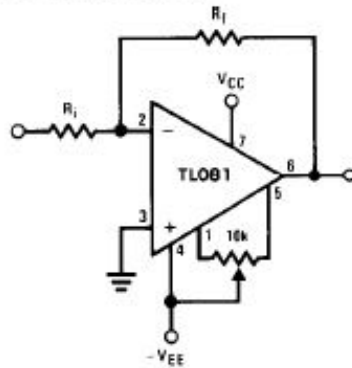


Simplified Schematic

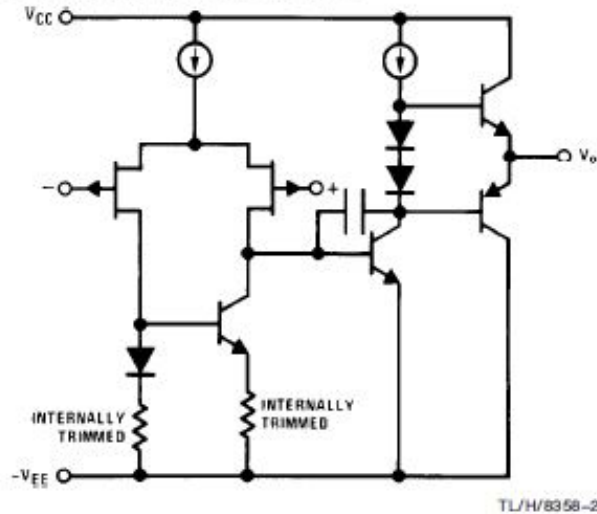


Connection Diagram

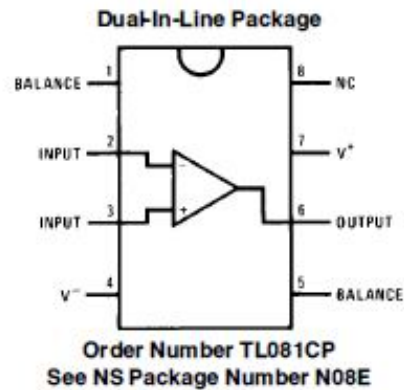

# VTB8440B photodiode

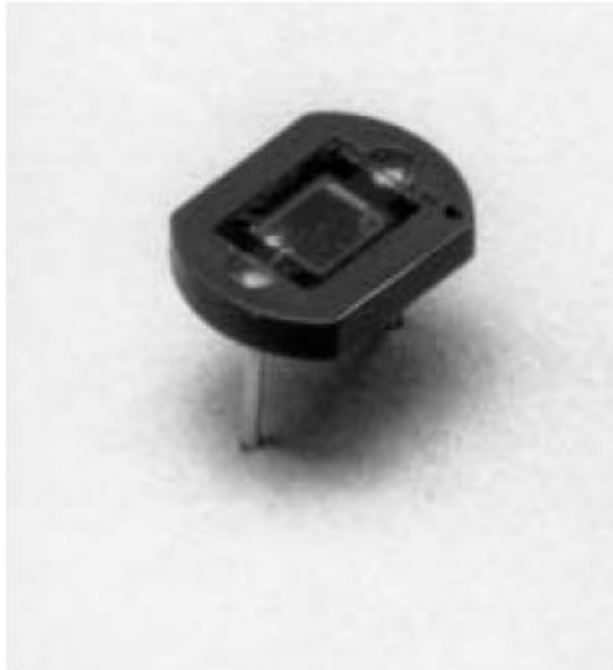

## PACKAGE DIMENSIONS inch (mm)

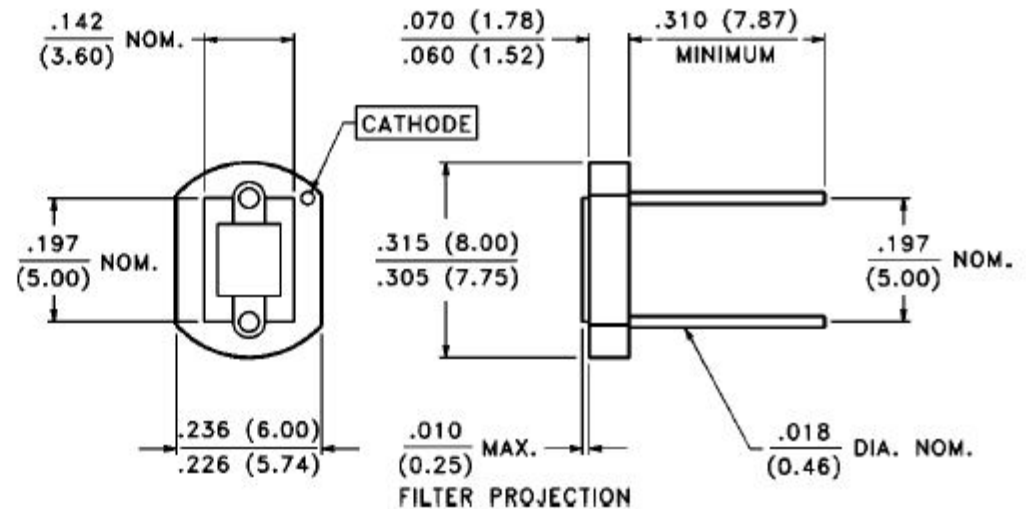

CASE 21F 8 mm CERAMIC  
CHIP ACTIVE AREA:  $.008 \text{ in}^2$  ( $5.16 \text{ mm}^2$ )



# VTB8440B photodiode

## ELECTRO-OPTICAL CHARACTERISTICS @ 25°C (See also VTB curves, pages 21-22)

SYMBOL	CHARACTERISTIC	TEST CONDITIONS	VTB8440B			VTB8441B			UNITS
			Min.	Typ.	Max.	Min.	Typ.	Max.	
$I_{SC}$	Short Circuit Current	H = 100 fc, 2850 K	4	5		4	5		$\mu A$
TC $I_{SC}$	$I_{SC}$ Temperature Coefficient	2850 K		.02	.08		.02	.08	%/°C
$V_{OC}$	Open Circuit Voltage	H = 100 fc, 2850 K		420			420		mV
TC $V_{OC}$	$V_{OC}$ Temperature Coefficient	2850 K		-2.0			-2.0		mV/°C
$I_D$	Dark Current	H = 0, VR = 2.0 V			2000			100	pA
$R_{SH}$	Shunt Resistance	H = 0, V = 10 mV		.07			1.4		G $\Omega$
TC $R_{SH}$	$R_{SH}$ Temperature Coefficient	H = 0, V = 10 mV		-8.0			-8.0		%/°C
$C_J$	Junction Capacitance	H = 0, V = 0		1.0			1.0		nF
$\lambda_{range}$	Spectral Application Range		330		720	330		720	nm
$\lambda_p$	Spectral Response - Peak			580			580		nm
$V_{BR}$	Breakdown Voltage		2	40		2	40		V
$\theta_{1/2}$	Angular Resp. - 50% Resp. Pt.			±50			±50		Degrees
NEP	Noise Equivalent Power		$1.1 \times 10^{-13}$ (Typ.)			$2.4 \times 10^{-14}$ (Typ.)			W/ $\sqrt{Hz}$
$D^*$	Specific Detectivity		$2.2 \times 10^{12}$ (Typ.)			$9.7 \times 10^{12}$ (Typ.)			cm $\sqrt{Hz}/W$


# VTB8440B photodiode
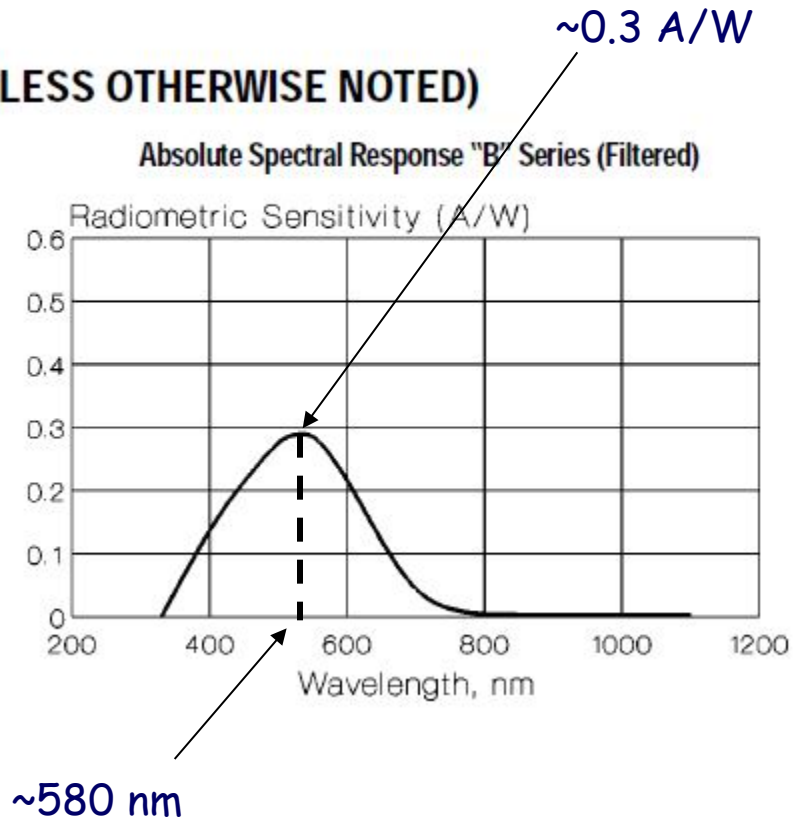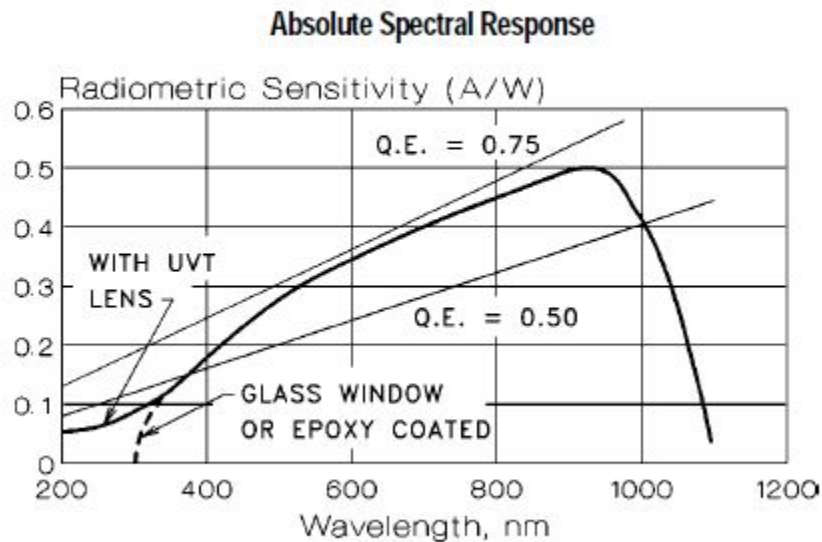
## TYPICAL CHARACTERISTIC CURVES @ 25°C (UNLESS OTHERWISE NOTED)





# Front panel

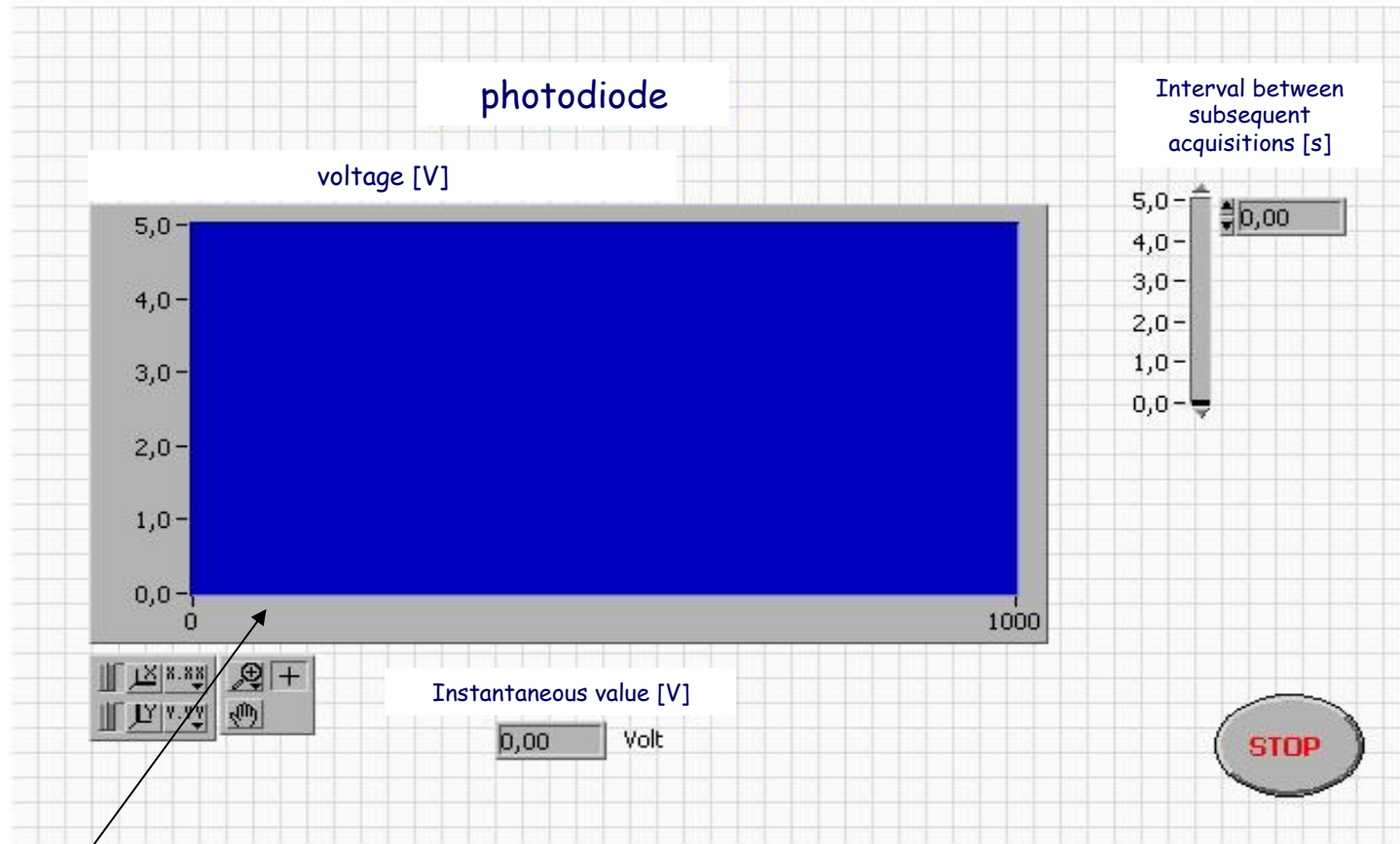


Waveform chart




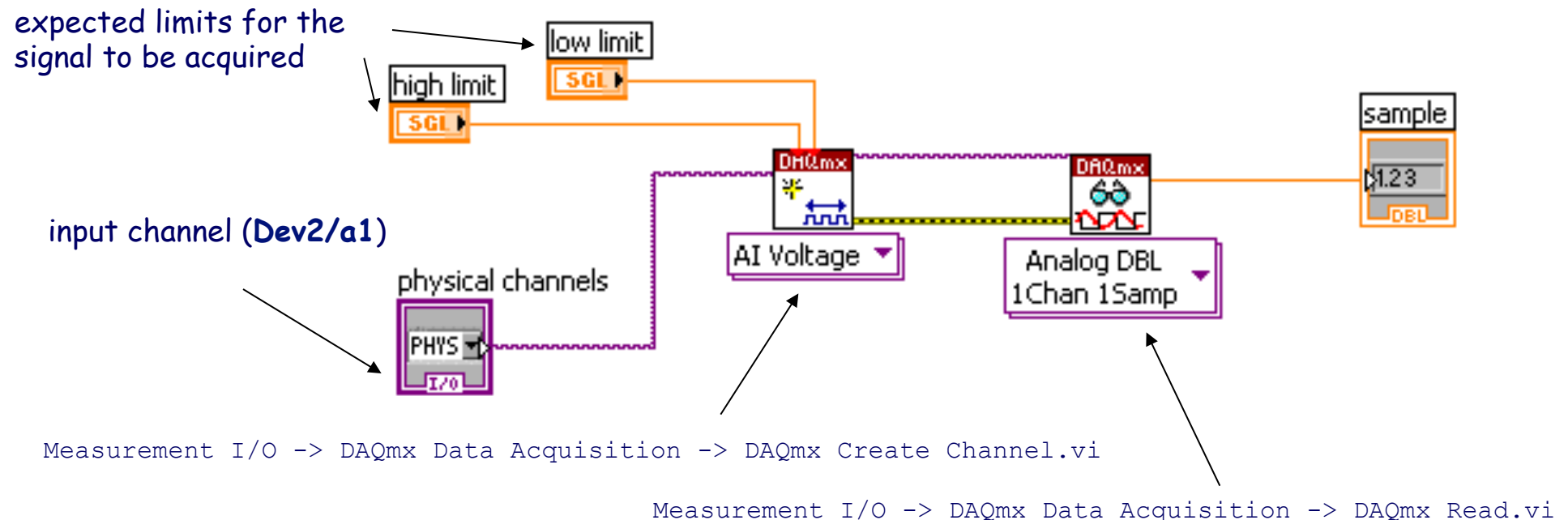
# DAQmx Create Channel.vi and DAQmx Read.vi

- DAQmx Create Channel.vi provides the acquisition board with information about the type and range of the signals to be acquired and about the input channel
- DAQmx Read.vi samples the signal from the specified channel and yield the measured value



# While loop


- Needed for continuous acquisition of the signal coming from the conditioning circuit (you can find it in the Structures menu from the Functions palette ) - a "stop" button should be included in the virtual instrument to stop the acquisition




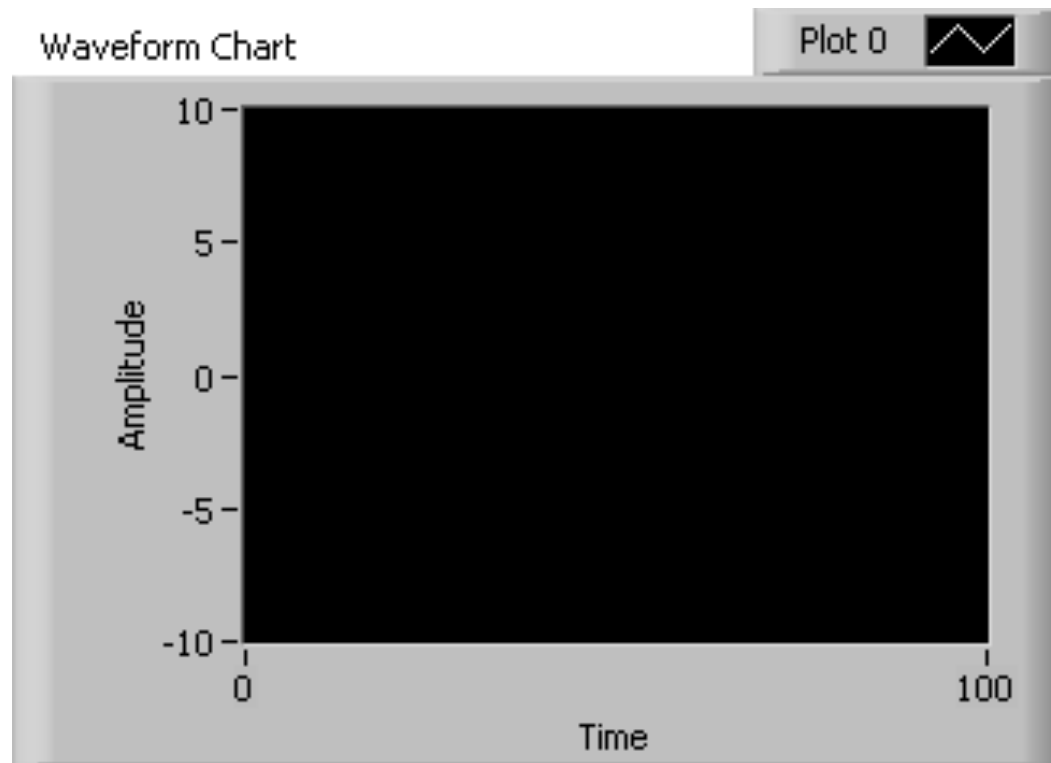
# Waveform chart


You can use a waveform chart for a graphical representation of the acquired data ('Graph' menu of the Controls palette, from the front panel window) - the acquired sample can be directly fed to the waveform chart



# For cycle

We can use a for cycle to reduce the effects of zero average disturbances, therefore improving the measurement accuracy

number of cycles

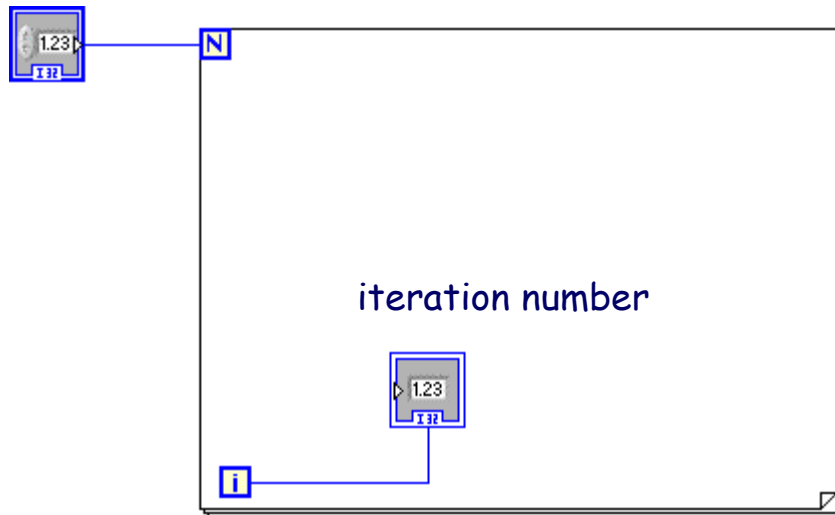

Instead of representing (in the graph or in the numeric indicator) each individual acquired sample of the signal, we can represent the average value of  $N$  samples - the speed at which the measurement result is represented on the graph will decrease by a factor of  $N$