




# Measuring the common emitter current gain $\beta$ in a bipolar junction transistor

---






# Measuring $\beta$

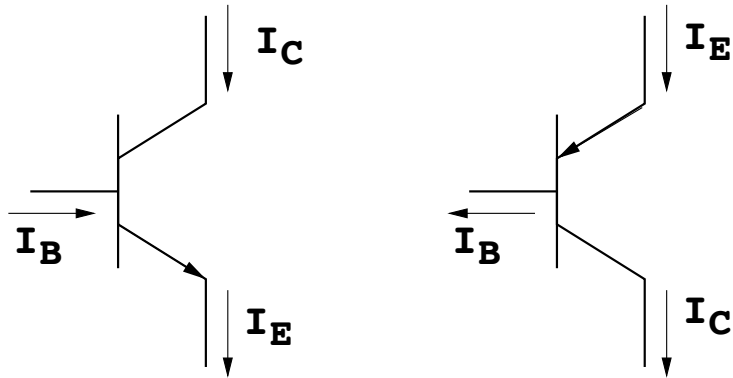

$$\beta(I_C, V_{CE}) = \frac{I_C}{I_B}$$

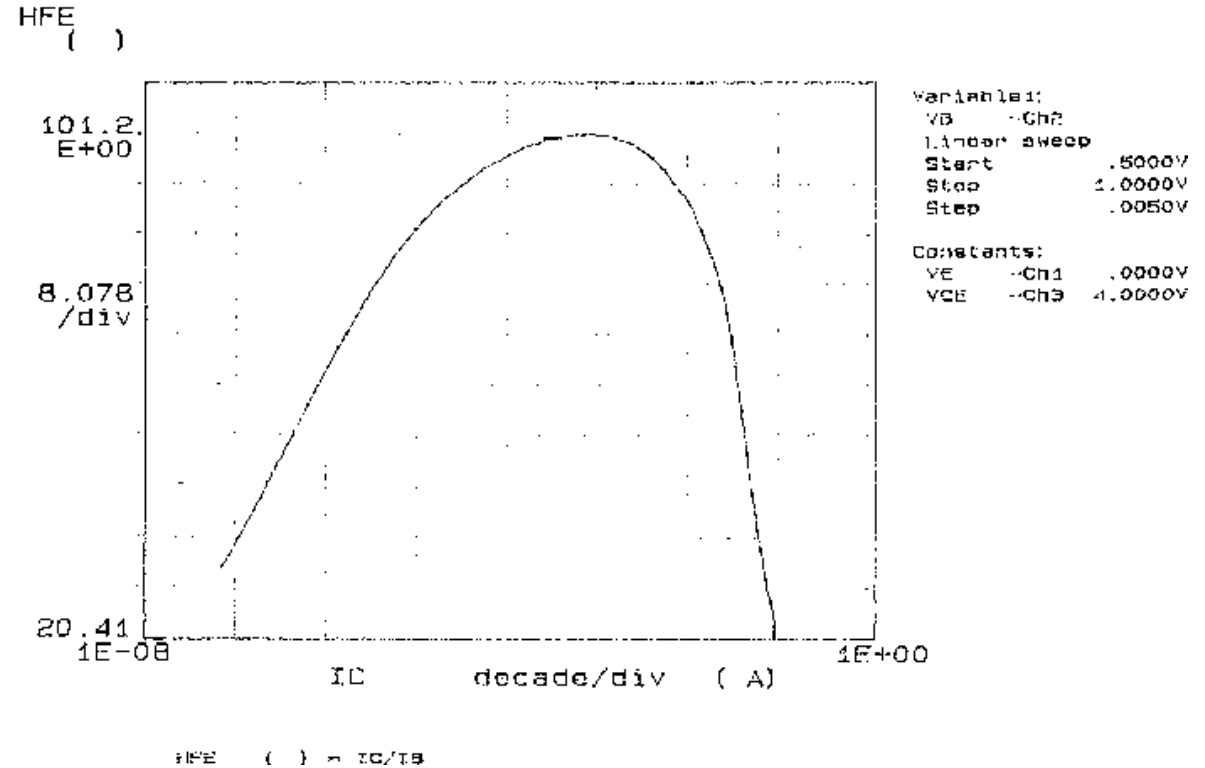\*\*\*\*\* GRAPHICS PLOT \*\*\*\*\*  
BFY90






# Purpose of the experiment

- Implementing a system allowing the user to measure the common emitter current gain  $\beta$  in NPN and PNP bipolar transistors. The system should include
  - a weighted resistor DAC controlling the collector current in the DUT (device under test)
  - a circuit setting the collector current of the transistor under test and  $V_{CB}=0$  (transistor in a diode connection)
  - a virtual instrument allowing the user to control the DAC, acquire the data relevant to the collector and base current in the DUT, compute  $\beta$  and represent it as a function of  $I_C$
- The virtual instrument should represent  $\beta$  as a function of  $I_C$  in graphical form and save the relevant data in the form of a table ( $I_C, \beta$ ) in a text file




# Measuring $\beta$

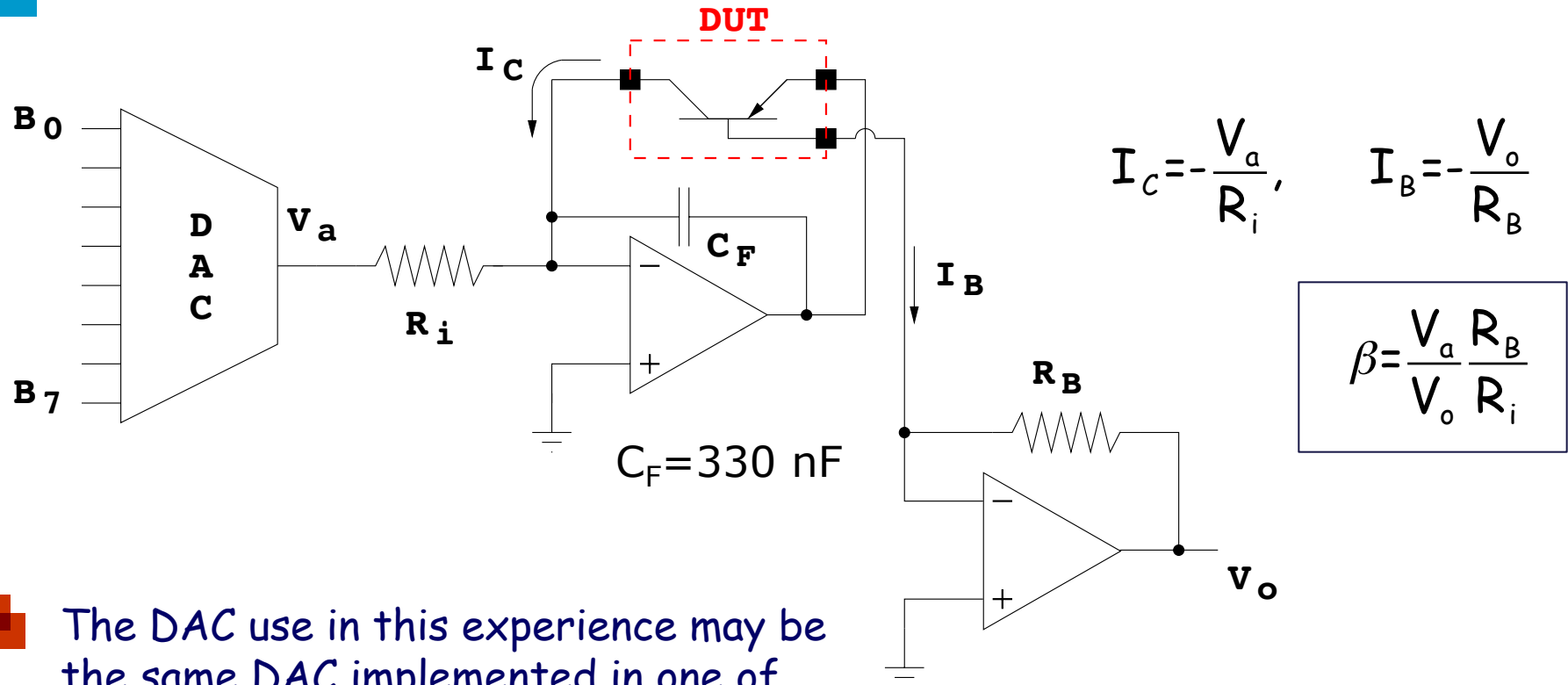

- The DAC use in this experience may be the same DAC implemented in one of the previous experiences
- $R_i$  should be chosen in such a way to have a maximum collector current of 10 mA;  $R_B$  should be chosen so that the voltage  $V_o$  at the output of the second amplifier covers the input dynamic range of the data acquisition board on the PC ( $\pm 10$  V)

# TL081 JFET input OpAmp

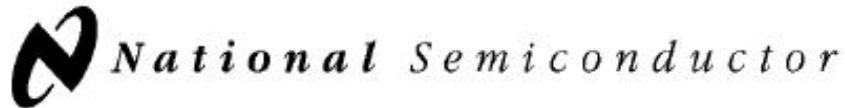

December 1995

## TL081 Wide Bandwidth JFET Input Operational Amplifier

### General Description

The TL081 is a low cost high speed JFET input operational amplifier with an internally trimmed input offset voltage (BI-FET II™ technology). The device requires a low supply current and yet maintains a large gain bandwidth product and a fast slew rate. In addition, well matched high voltage JFET input devices provide very low input bias and offset currents. The TL081 is pin compatible with the standard LM741 and uses the same offset voltage adjustment circuitry. This feature allows designers to immediately upgrade the overall performance of existing LM741 designs.

The TL081 may be used in applications such as high speed integrators, fast D/A converters, sample-and-hold circuits and many other circuits requiring low input offset voltage, low input bias current, high input impedance, high slew rate and wide bandwidth. The devices has low noise and offset voltage drift, but for applications where these requirements

are critical, the LF356 is recommended. If maximum supply current is important, however, the TL081C is the better choice.


### Features

■ Internally trimmed offset voltage	15 mV
■ Low input bias current	50 pA
■ Low input noise voltage	25 nV/ $\sqrt{\text{Hz}}$
■ Low input noise current	0.01 pA/ $\sqrt{\text{Hz}}$
■ Wide gain bandwidth	4 MHz
■ High slew rate	13 V/ $\mu\text{s}$
■ Low supply current	1.8 mA
■ High input impedance	$10^{12}\Omega$
■ Low total harmonic distortion $A_V = 10$ , $R_L = 10\text{k}$ , $V_O = 20\text{ Vp-p}$ , $\text{BW} = 20\text{ Hz} - 20\text{ kHz}$	<0.02%
■ Low 1/f noise corner	50 Hz
■ Fast settling time to 0.01%	2 $\mu\text{s}$




# TL081 JFET input OpAmp

Typical Connection

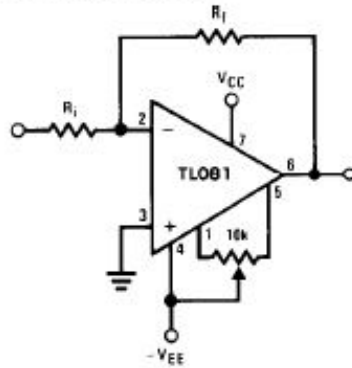


Simplified Schematic

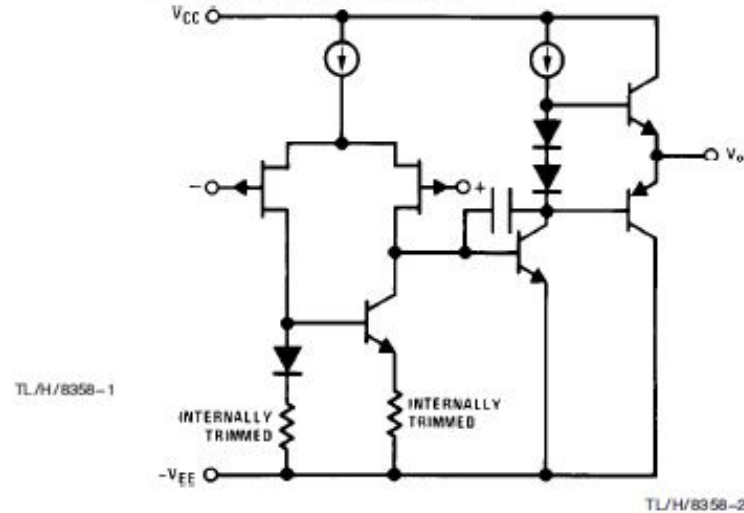


Connection Diagram

Dual-In-Line Package

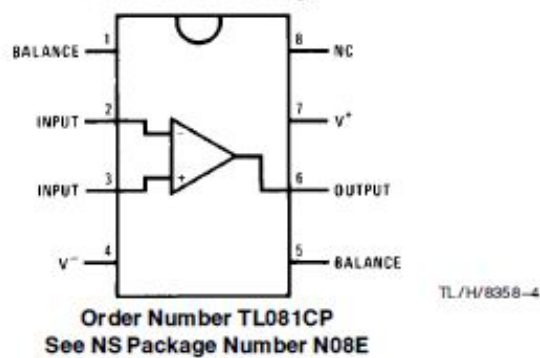
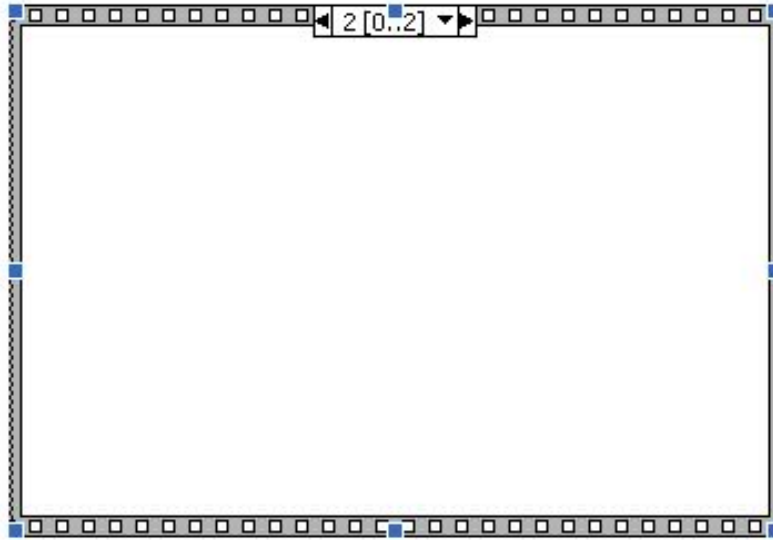
# Virtual Instrument

As far as the block diagram is concerned, the LabVIEW VI can be implemented by means of a sequence structure including 4 frames (to add a frame, right click on the frame of the structure and select "Add Frame After"). The sequence structure makes it possible to execute a set of instructions according to a user defined time sequence (first the instructions included in frame 0 are executed, then those included in frame 1, etc.)




The only purpose of using this structure is that of introducing a clear time separation between the four tasks of the program:

- **DAC programming** (frame #0)
- **acquisition of  $V_a$**  (frame #1)
- **acquisition of  $V_o$**  (frame #2)
- **calculation and graphical representation of beta** (frame #3)

# Measuring $\beta$ as a function of $I_c$

In order to measure the value of beta for different values of the collector current, the sequence structure can be included in a for loop with 256 iterations, one for each of the possible DAC output levels

number of cycles

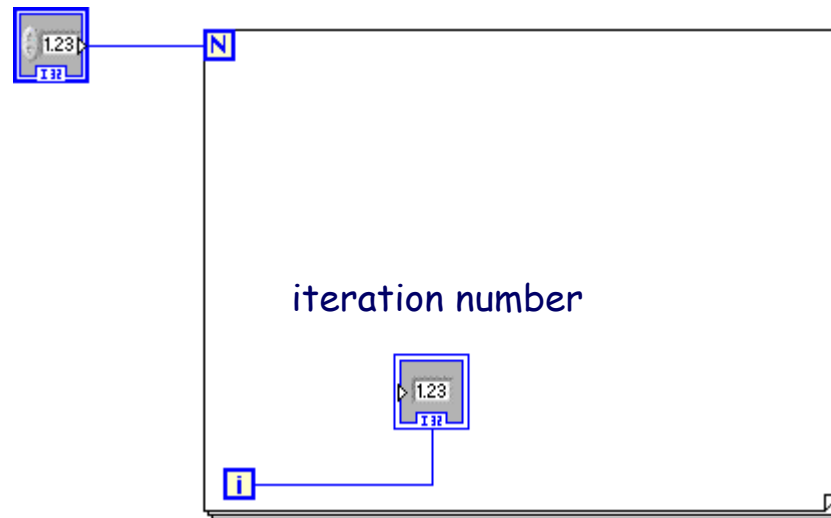




# DAC programming (frame #0)

- DAQmx Create Channel.vi is used to configure the digital channel of the data acquisition board (DAQ, on the PC)
- DAQmx Write.vi is used to set the value at the digital output channels configured by the previous function

specifies the name of the digital lines or the ID number of the ports used to create the virtual channel (Dev1/port0/line0:7)

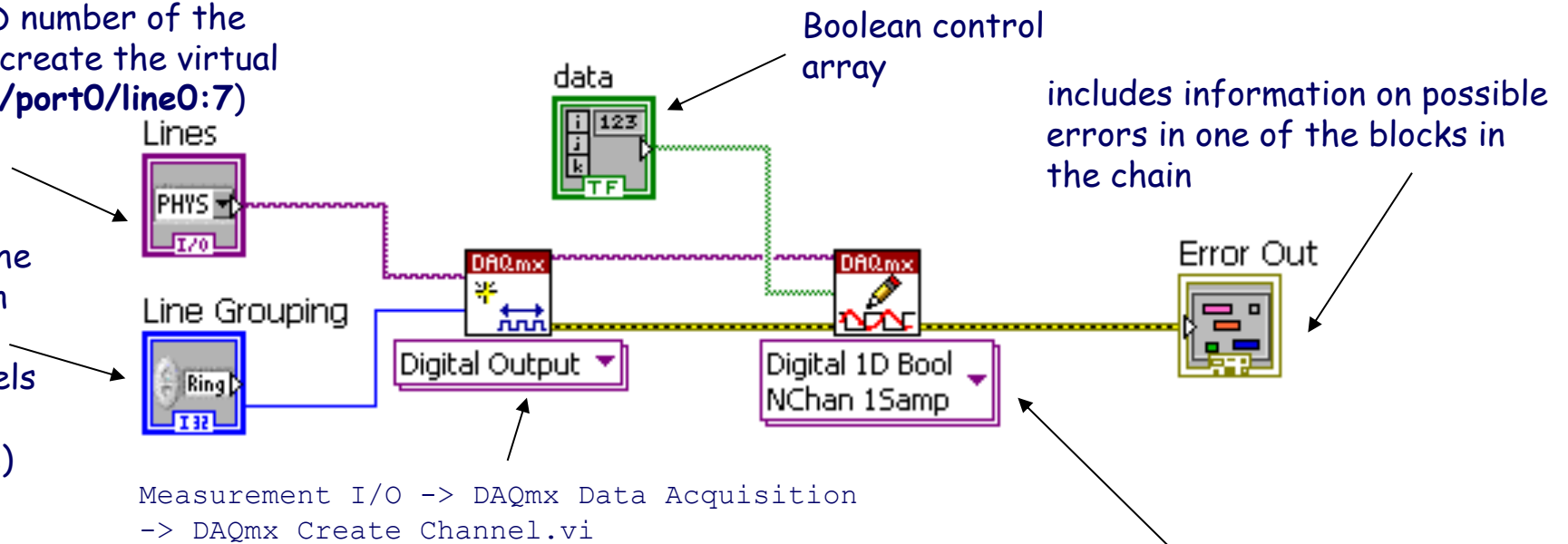
grouping of the digital lines in one or more virtual channels (one channel for each line)



Measurement I/O -> DAQmx Data Acquisition -> DAQmx Write.vi

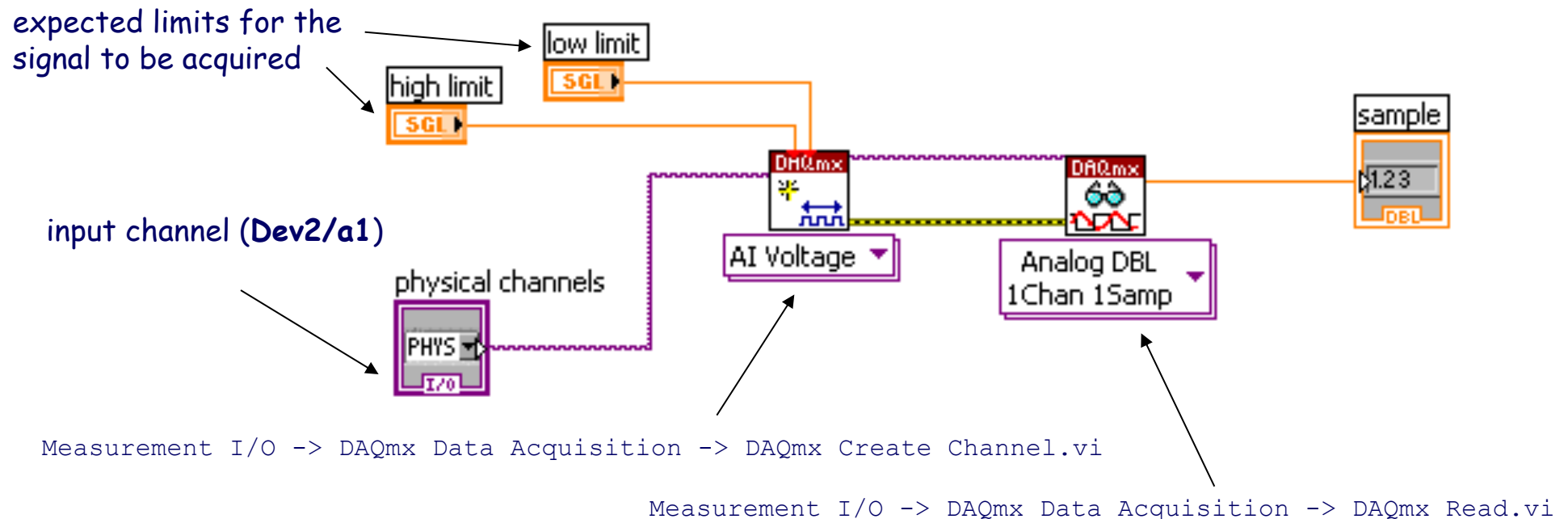
# Acquiring $V_a$ e $V_o$ (frame #1 and #2)

- DAQmx Create Channel.vi provides the acquisition board with information about the type and range of the signals to be acquired and about the input channel
- DAQmx Read.vi samples the signal from the specified channel and yield the measured value




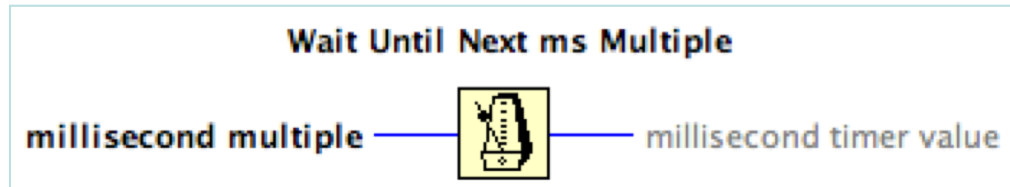
# Acquisition Timing


Before acquiring  $V_o$ , one should wait for the currents in the DUT to reach the regime conditions. For this purpose, a timing function should be used in the first frame of the sequence structure



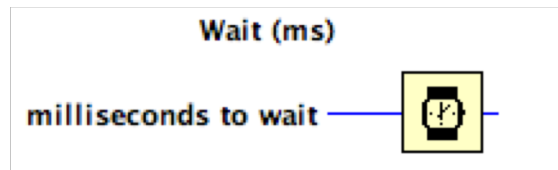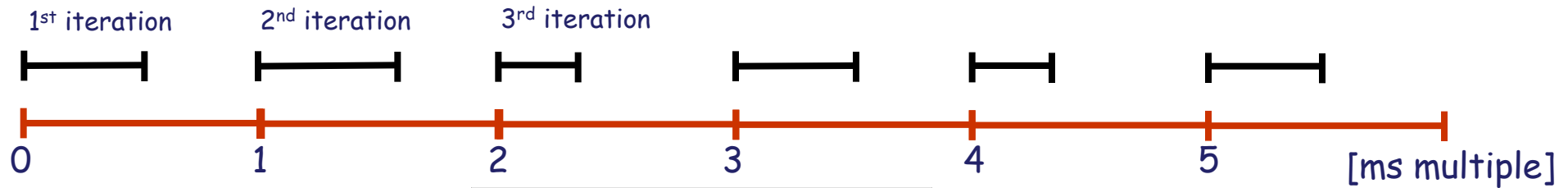Waits until the timer content is a multiple of "millisecond multiple" before starting an iteration - generally used to synchronize the loop execution with the system clock



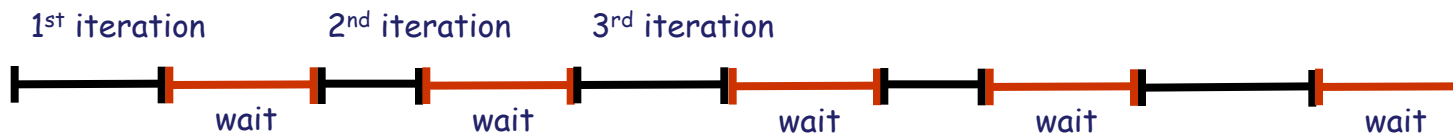Waits for the specified number of milliseconds before starting an iteration






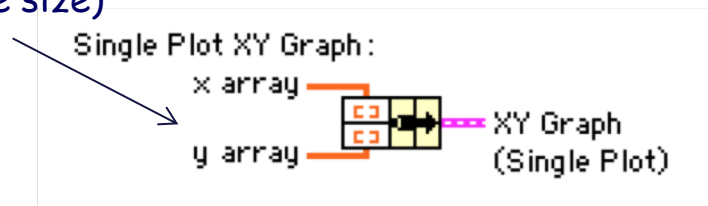
# Graphical representation of $\beta(I_c)$

- XY graph (Modern  $\rightarrow$  Graph -  
 $\rightarrow$  XY Graph o Classic  $\rightarrow$  Classic Graph  
 $\rightarrow$  XY Graph)
- A Bundle function is required  
(Programming  $\rightarrow$  Cluster, Class &  
Variant  $\rightarrow$  Bundle) to group the  
independent (X) and dependent  
(Y) variables in a single array

Input data in the form of  
vectors (same size)



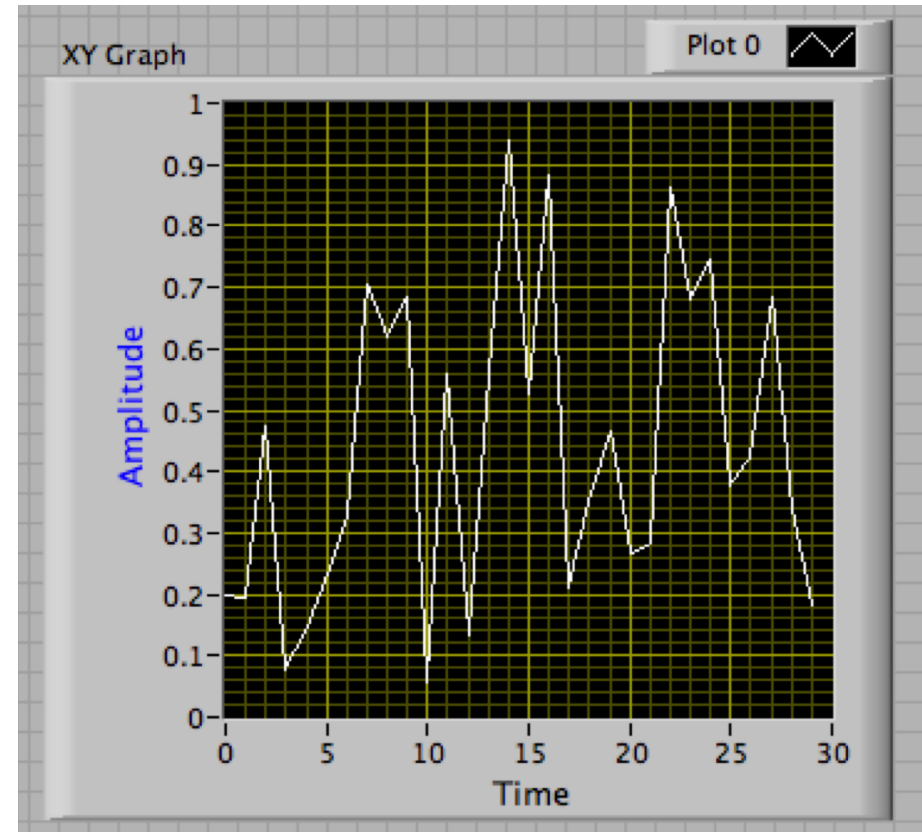
Suggestion: to generate the data vectors  
one could use tunnels in "indexed" modes in a  
for structure




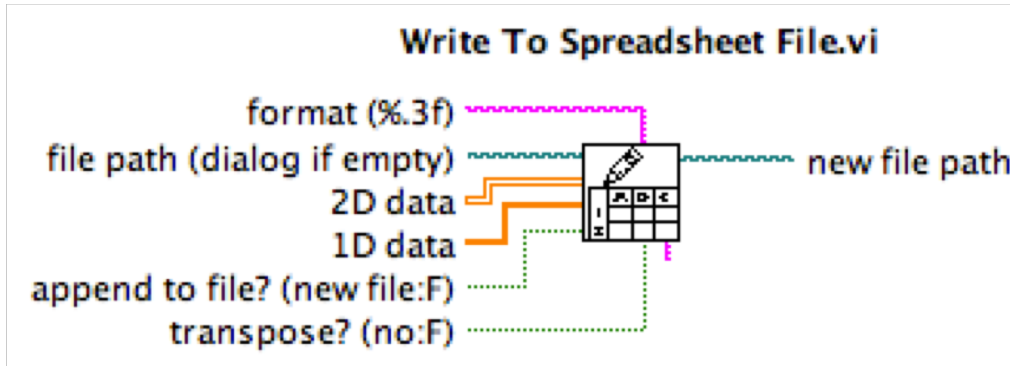
# Writing a file


Programming-> File I/O->  
Write To Spreadsheet File.vi



output: 1 2D array (2  
column data table)

input: 2 1D arrays


Programming-> Array-> Build  
Array

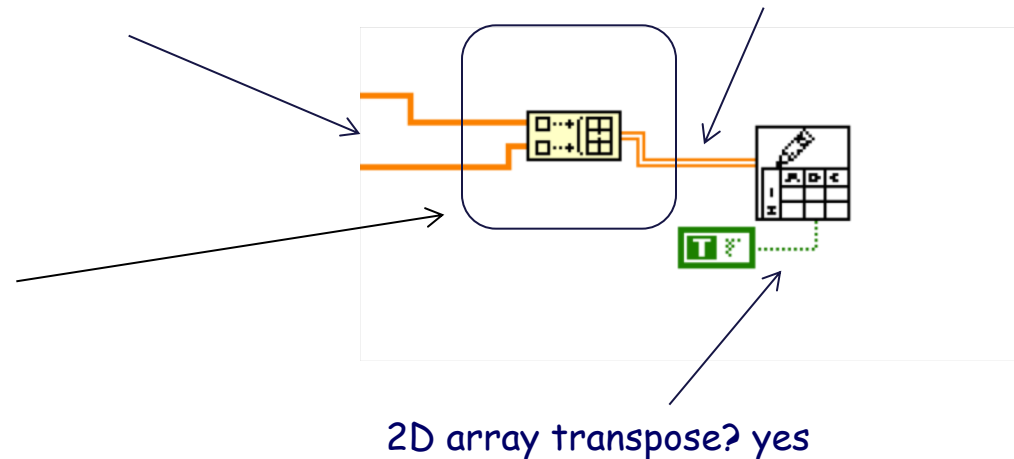

# FOR cycle for noise rejection

- We can use a for cycle to reduce the effects of zero average disturbances, therefore improving the measurement accuracy

number of cycles

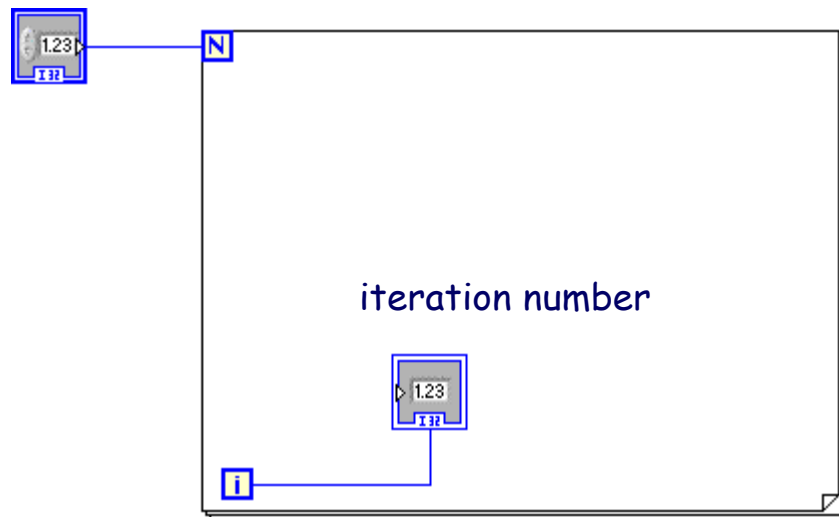

- Instead of representing (in the graph or in the numeric indicator) each individual acquired sample of the signal, we can represent the average value of N samples - the speed at which the measurement result is represented on the graph will decrease by a factor of N